
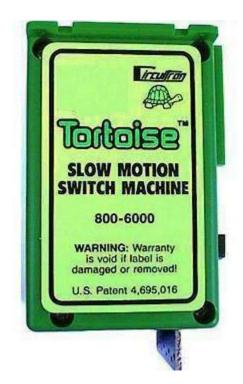
# How To Wire Your Tortoise Switch Machine




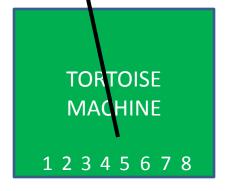Ron St.Laurent NMRA NCR Capital Division 5 Lansing Model Railroad Club





Simple DC connections for a Tortoise is to connect one wire to terminal 1 and one wire to terminal 8.

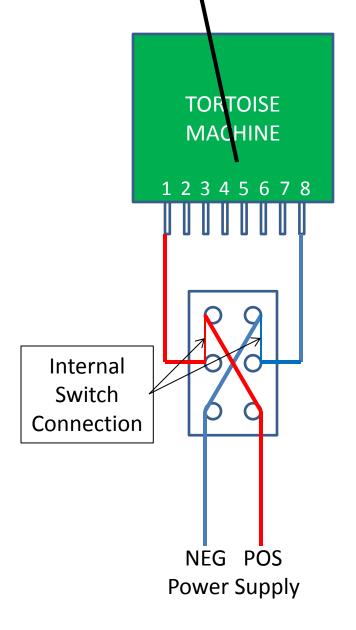Reversing polarity on terminals 1 and 8 will change the direction of the switch machine.




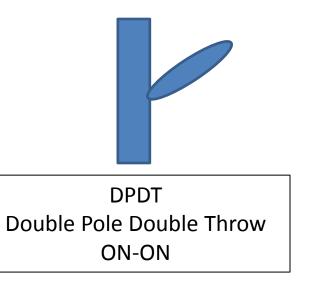Reversing polarity on terminals 1 and 8 will change the direction of the switch machine.




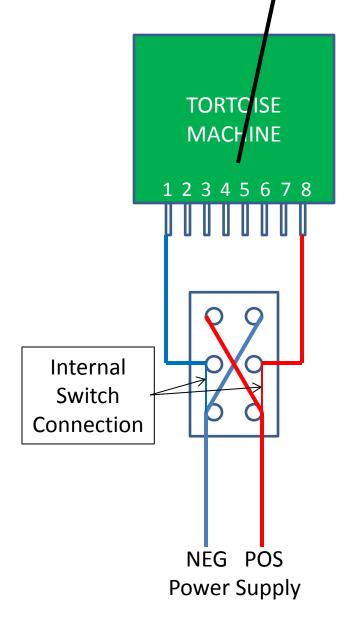


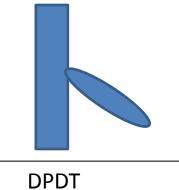Reversing polarity on terminals 1 and 8 will change the direction of the switch machine.





Double Pole Double Throw ON-ON

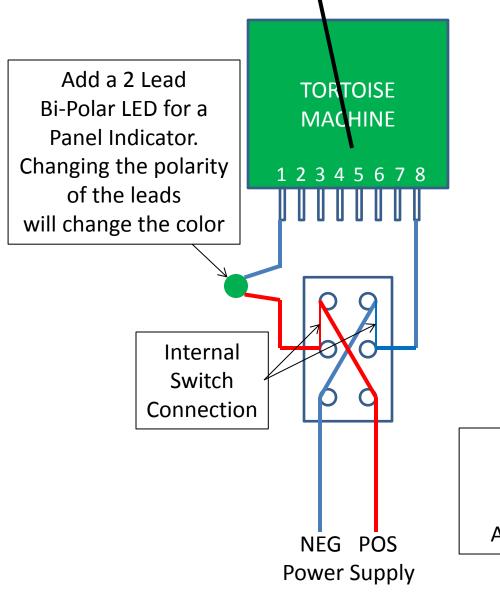

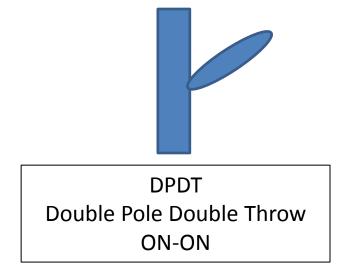


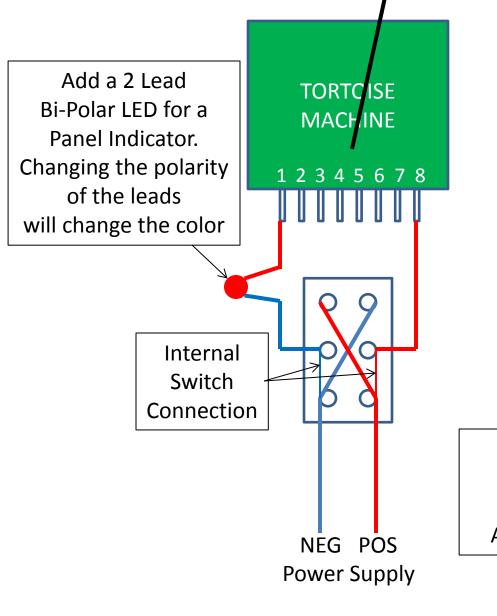
Good practice is to make "up" your normal traffic flow. One glance down the fascia And you know you're set for the Main.



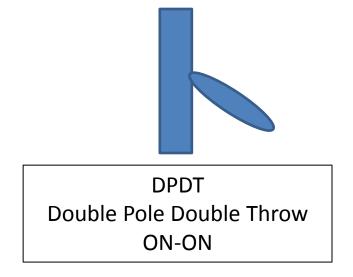


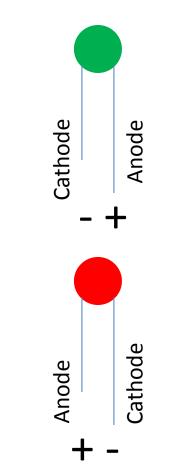Good practice is to make "up" your normal traffic flow. One glance down the fascia And you know you're set for the Main. Bi-Polar LEDs are two LEDs inside one package. Leads serve as both Anode and Cathode.




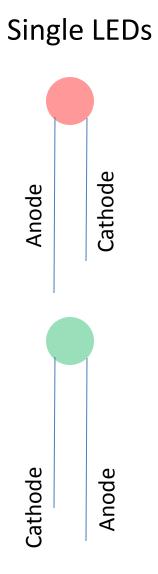


#### Single LEDs

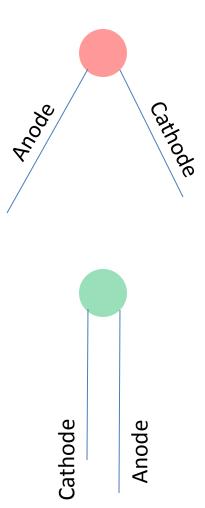

#### Single LEDs

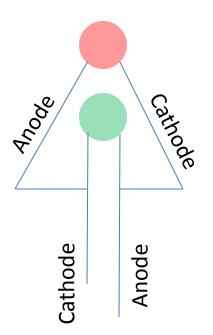

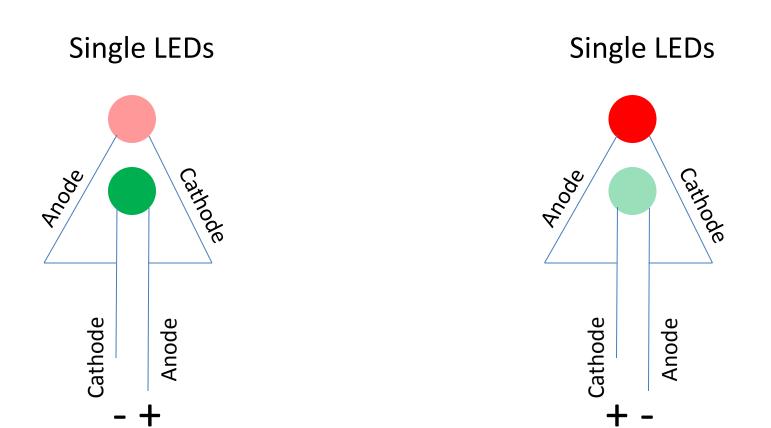



## A good, inexpensive, source for toggle switches. DPDT ON-ON is 75 cents. In quantities of 100, 65 cents.



XXXXX DPDT ON-ON Mini Toggle Switch Item #: 31886 SW \$0.75

PavPa



**DPDT On-Momentary Mini Toggle** Switch Item #: 16073 SW \$0.69




DPDT Momentary-Off-Momentary Mini Toggle Switch, UL Item #: 25016 SW \$0.79



DPDT On-Off-Momentary Mini **Toggle Switch** Item #: 16074 SW \$0.69
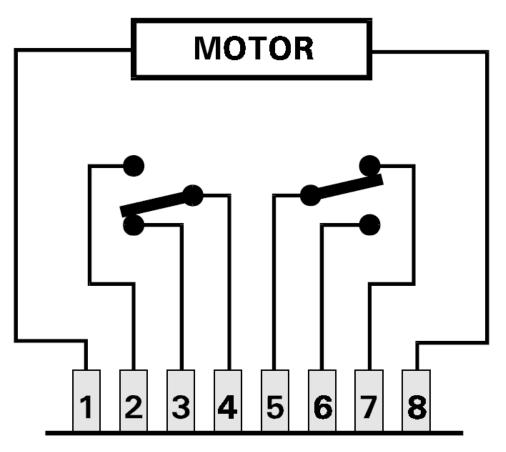
### Internal connections of the Tortoise with 2 SPDT Switches



If you wish to power your frogs use one of the internal SPDT switches built into the Tortoise.

FIGURE 2.

# Questions?

Ron St.Laurent NMRA NCR Capital Division 5 Lansing Model Railroad Club